



Electronic Circuits and Communication Fundamentals

DEC 18

Computer Engineering (Semester 3)

Total marks: 80

Total time: 3 Hours

INSTRUCTIONS

- (1) Question 1 is compulsory.
- (2) Attempt any **three** from the remaining questions.
- (3) Draw neat diagrams wherever necessary.

1.a. Explain the concept and significance of CMRR and slew Rate in case of op-amps. (5 marks)

1.b. Given $\beta\beta = 120$ and $I_{EIE} = 3.2 \text{ mA}$ for a common-emitter configuration with $r_{0r0} = \infty \infty \Omega\Omega$, determine.

i) $Z_i Z_i$

ii) $A_v A_v$ if a load of $2 \text{ k}\Omega$ is applied.

iii) $A_i A_i$ with the $2 \text{ k}\Omega$ load. (5 marks)

1.c. Discuss the factors that influence modulation index of an FM wave. (5 marks)


1.d. Justify that adaptive delta modulation superior to delta modulation. (5 marks)

2.a. The emitter bias configuration as shown in following figure has the specifications:

$I_{CQ} I_{CQ} = 12 I_{Csat} 12 I_{Csat}$ $I_{Csat} I_{Csat} = 8 \text{ mA}$

$V_{CVC} = 18 \text{ V}$ and $\beta\beta = 110$

Determine R_{CRC} , R_{ERE} and R_{aRa}

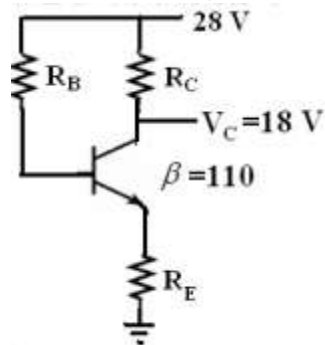

(10 marks)



2.b. Explain how op-amp can be used comparator and zero crossing detector.
(10 marks)

3.a. What is the source of the leakage current in a transistor?

If the emitter current of a transistor is 8 mA and I_{BIB} is $1/100$ of I_{CIC} determine the levels of I_{CIC} and I_{BIB} .

(5 marks)


3.b. Draw and explain Colpitts oscillator.

(5 marks)

3.c. Explain principle of FDM.

(5 marks)

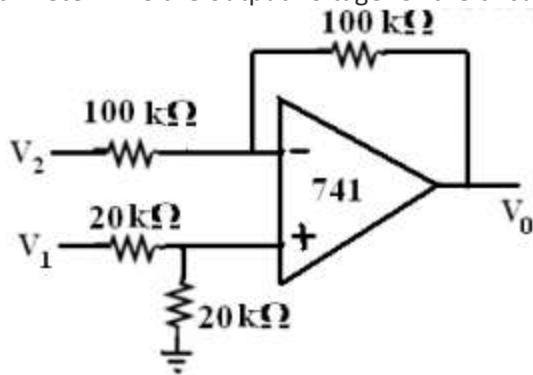3.d. Determine the output voltage for the circuit if $V_1 = 5V$, and $V_2 = 3V$



(5 marks)

4.a. What is DSBSC wave and explain its generation using balanced modulator.
(10 marks)

4.b. What is multiplexing in communication system? Draw block diagram of TDM-PCM system and explain.

(10 marks)

5.a. State Shannon's theorem on channel capacity.

What is the maximum capacity of a perfectly noiseless channel whose bandwidth is 120 Hz, which the values of the data transmitted may be indicated by any one of the 10 different amplitudes?

(10 marks)

5.b. With respect to neat diagram explain the elements of analog communication system,.

(10 marks)

6.a. What is meant by Nyquist rate in sampling and explain its significance.

(5 marks)

6.b. Give the proper definition for entropy and information rate.

(5 marks)

6.c. Write short note on op-amp as differentiator.

(5 marks)

6.d. Differentiate between Class A and Class C power amplifiers with respect to circuit diagram, operating cycle and power efficiency.

(5 marks)