



Electronic Circuits and Communication Fundamentals

MAY 18

Computer Engineering (Semester 3)

Total marks: 80

Total time: 3 Hours

INSTRUCTIONS

- (1) Question 1 is compulsory.
- (2) Attempt any **three** from the remaining questions.
- (3) Draw neat diagrams wherever necessary.

1.a. Draw input and output characteristics of BJT.

State significance of DC load line.

(5 marks)

1.b. For an AM DSBFC modulator with carrier frequency $f_c = 100\text{kHz}$ and a maximum modulating signal frequency $f_m = 5\text{kHz}$, determine

- i) Frequency limit for the upper and lower sidebands
- ii) Bandwidth
- iii) Draw the frequency spectrum

(5 marks)

1.c. Write a note on zero crossing detector using op-amp with waveforms.

(5 marks)

1.d. Compare Class A and Class C Amplifiers.

(5 marks)

2.a. Explain Superhetrodyne receiver with suitable diagram


(5 marks)

2.b. Implement summing Operational Amplifiers using inverting configuration of Op-amp.

(5 marks)

2.c. For the emitter bias network of figure below, determine :

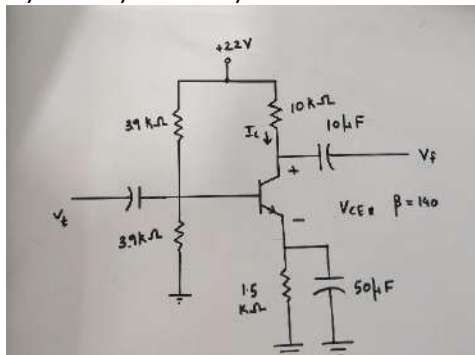- i) I_b ii) I_c iii) V_{ce}
- iv) V_c v) E_{th} vi) R_{th}



(10 marks)



- 3.a.** Explain generation of DSBSC using balanced Modulator along with its frequency and power spectrum. (10 marks)
- 3.b.** With suitable waveforms explain how Op-amp can be used as Differentiator. (10 marks)
- 4.a.** For an AM DSBFC envelope with $V_{max} = 20V$ and $V_{min} = 4V$; determine
- Peak amplitude of USF AND LSF
 - Peak amplitude of carrier
 - Peak change in the amplitude of the envelope
 - Modulation coefficient
 - Draw the AM envelope. (10 marks)
- 4.b.** Differentiate between TDM and FDM (5 marks)
- 4.c.** State Shannon's theorem and explain its significance. (5 marks)
- 5.a.** Draw PAM, PWM and PPM waveforms in time domain using a sinusoidal signal and explain in brief. (10 marks)
- 5.b.** Define and explain in brief Amount of information, average information, information rate and channel capacity of a communication system. (10 marks)
- 6.a.** State significance of modulation in communication. (5 marks)
- 6.b.** Write a note on pulse code modulation with waveforms (5 marks)
- 6.c.** Explain and give ideal values of following parameters of an op-amp:
- CMRR
 - slew rate
 - offset voltage
 - Input Resistance
 - Output Impedance (10 marks)