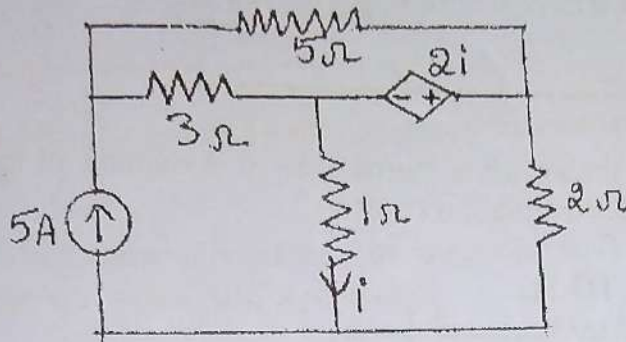





- I.B : 1. Question No. 1 is compulsory.  
 2. Attempt any three from the remaining questions.

02 JUN 2018


- a) Find the voltage drop across  $5\Omega$  resistor in the circuit given below. 5



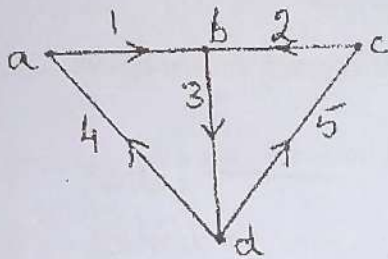- (b) For the graph given below obtain the incidence matrix and find the number of possible trees. 5



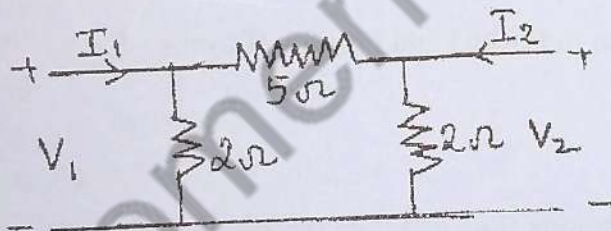
- (c) Find y parameters for the two-port network shown in figure. 5



- (d) Check whether the following polynomials are Hurwitz 5

- (i)  $P(s) = s^4 + 7s^3 + 6s^2 + 21s + 8$   
 (ii)  $P(s) = s^5 + 2s^3 + s$

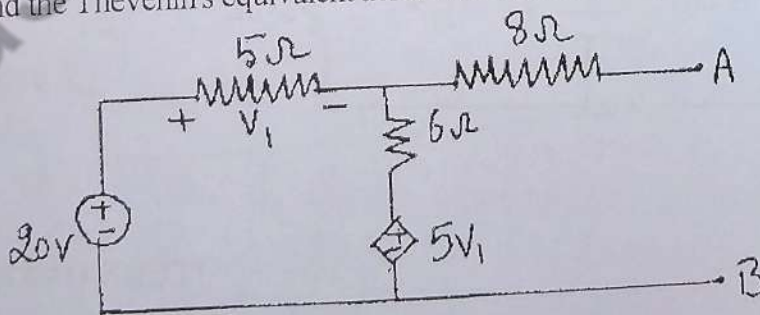
- (a) Find the Thevenin's equivalent across AB and find the power dissipated in a  $25\Omega$  load. 10




[TURN OVER

(b) Find h parameters for the following Two-port network.

5

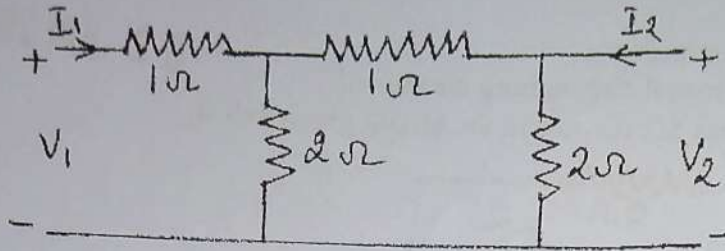

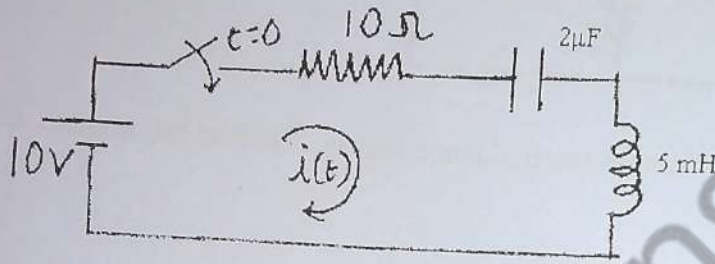(c) In the network shown below the switch is closed at  $t = 0$ . Assuming all initial conditions to be zero, find  $i$ ,  $di/dt$ ,  $d^2i/dt^2$  for  $t = 0^+$ .



3. (a) Find the tie-set and f-cutset matrix for the oriented graph shown below.

10




(b) Realize the following function in Foster I and Foster - II forms.

10

$$Z(s) = \frac{(s+1)(s+4)}{s(s+2)}$$

4. (a) A switch is in position A for a long time and then thrown to position B at  $t = 0$ . Find  $i(t)$  for  $t > 0$ . At what value of 't' the current  $i(t)$  will become half of current at  $t = 0$

10

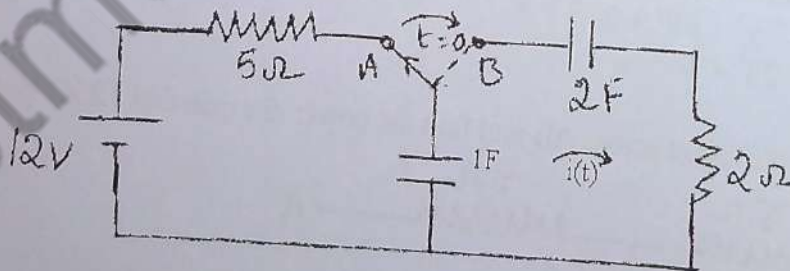


[TURN OVER




For the following network find the driving point impedance function.

5

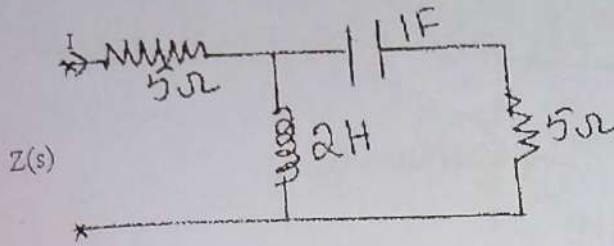

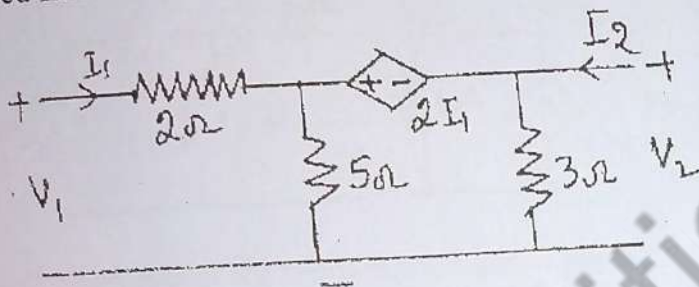- ) Find the condition for symmetry and reciprocity for a two port network using any one parameter. 5
- a) Obtain the ABCD parameters of the following network. If two such networks are cascaded find the overall ABCD parameter. 10




- (b) Check whether the following function is positive real or not. 5

$$F(s) = \frac{(s^2 + 6s + 5)}{(s^2 + 9s + 14)}$$

- (c) Find the oriented graph if the incidence matrix of the network is as given below. 5

$$A = \begin{bmatrix} 1 & 0 & 0 & 1 & 1 & 0 & 0 \\ 0 & -1 & 1 & 0 & -1 & 0 & 0 \\ -1 & 1 & 0 & 0 & 0 & 0 & -1 \\ 0 & 0 & 0 & -1 & 0 & 1 & 0 \end{bmatrix}$$

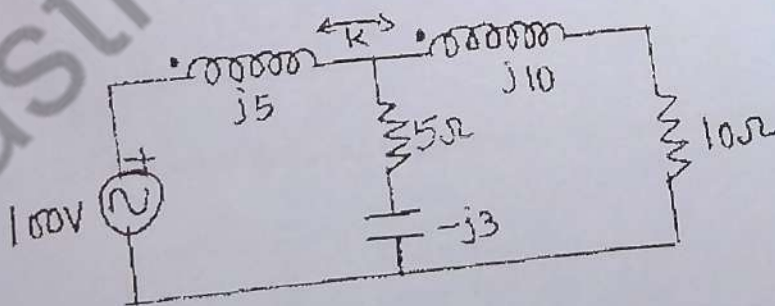6. (a) Find the mesh currents if the coupling factor  $k = 0.6$  10



[TURN OVER

(b) Find  $i_2(t)$  using Laplace transform.

10

