

**GUJARAT TECHNOLOGICAL UNIVERSITY****BE - SEMESTER– III (New) EXAMINATION – WINTER 2019****Subject Code: 3130906****Date: 28/11/2019****Subject Name: Electrical Circuit Analysis****Time: 02:30 PM TO 05:00 PM****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

		<b>MARKS</b>
<b>Q.1</b>	(a) State and explain Reciprocity theorem.	<b>03</b>
	(b) State and explain Maximum power transfer theorem with suitable example.	<b>04</b>
	(c) Obtain Thevenin's equivalent resistance of the circuit given in fig.1 to the left of the terminals a-b.	<b>07</b>
<b>Q.2</b>	(a) In the fig.2, the switch k is first kept at position 1 and steady state condition is reached. At $t = 0$ , switch is moved to position 2. Find the current in both the cases.	<b>03</b>
	(b) Explain time constant in case of series R-L and series R-C circuit.	<b>04</b>
	(c) In the fig.3, the switch is closed at $t = 0$ . Find value of $i$ , $di/dt$ , $d^2i/dt^2$ at $t=0^+$ . Assume initial current of inductor to be zero.	<b>07</b>
	<b>OR</b>	
	(c) Explain in detail about transient response in series R-C circuit having DC excitation.	<b>07</b>
<b>Q.3</b>	(a) Explain the importance of Dot convention in coupled circuit with suitable example.	<b>03</b>
	(b) Draw impedance triangle and explain related terms.	<b>04</b>
	(c) For the network shown in fig.4, find the node current I using node voltage technique.	<b>07</b>
	<b>OR</b>	
<b>Q.3</b>	(a) In the fig.5, an unknown impedance of $Z \Omega$ is connected in series with $(5 + j8) \Omega$ coil. If $I = 2.5 \angle -15^\circ$ A, find value of Z.	<b>03</b>
	(b) Find the current in a series R-L circuit having $R = 2 \Omega$ and $L = 10$ H while a DC voltage of 100 V is applied. What is the value of this current after 5 seconds of switching on?	<b>04</b>
	(c) The circuit shown in fig.6 is operating in the sinusoidal steady state. Find $I_1$ and $I_2$ by loop analysis and determine ratio $V_0 / V_s$ . Assume $\omega = 10^3$ rad / sec.	<b>07</b>
<b>Q.4</b>	(a) Find driving point impedance of the given network shown in fig.7.	<b>03</b>
	(b) Find inverse Laplace of given $F(s)$ . $F(s) = \frac{(s+2)}{s(s+3)(s+4)}$	<b>04</b>
	(c) Obtain the step response for the R-L series circuit shown in fig.8.	<b>07</b>

**OR**

- Q.4** (a) Explain characteristics of unit ramp function. **03**  
 (b) Determine the transfer function  $H(s) = V_0(s) / I_0(s)$  of the circuit in fig.9. **04**  
 (c) Find  $v_0(t)$  in the circuit of fig.10, assuming zero initial condition. **07**
- Q.5** (a) What is the condition of symmetry of all different two port parameters? **03**  
 (b) Briefly describe h parameters for a two port network. **04**  
 (c) Obtain Z-parameters of the circuit shown in fig.11. **07**
- OR**
- Q.5** (a) Find Y-parameters of the circuit shown in fig.12 **03**  
 (b) Derive expression of ABCD parameters in terms of Z parameters. **04**  
 (c) Determine Z-parameters of the circuit shown in fig.13. **07**

\*\*\*\*\*



